

ELECTRICAL ENERGY IN THE HOME QUIZ

1. A conductor has a resistance of 20Ω . Given that its length is doubled and the radius of its cross-sectional area is also doubled, what is its new resistance? (3 marks)

$$R_{\text{orig}} = \frac{L}{A} = \frac{L}{\pi r^2} = 20\Omega$$


$$\begin{aligned} R_{\text{new}} &= \frac{2L}{\pi(2r)^2} \\ &= \frac{2L}{4\pi r^2} \\ &= \frac{1}{2} R_{\text{orig}} \\ &= \frac{1}{2} \times 20 \\ &= 10\Omega \# \end{aligned}$$

2. A current of $3A$ flows for a period of 1.5 seconds. How many coulombs of charge and hence how many electrons pass a given point in this time? (2 marks)

$$\begin{aligned} I &= 3A \\ t &= 1.5 \text{ seconds} \\ q &=? \\ n &=? \\ e &= 1.6 \times 10^{-19} C \\ I &= \frac{q}{t} \\ q &= It \\ &= 3 \times 1.5 \\ &= 4.5 C \# \end{aligned}$$

$$\begin{aligned} q &= ne \\ n &= \frac{q}{e} \\ &= \frac{4.5}{1.6 \times 10^{-19}} \\ &= 2.8 \times 10^{19} e^- \# \end{aligned}$$

3.

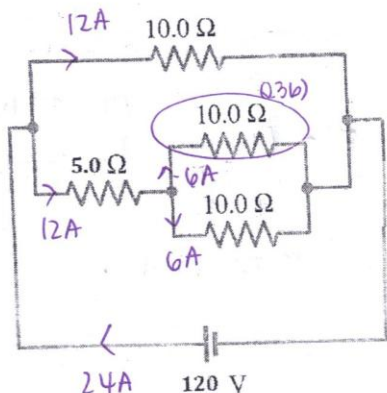

- a) Calculate the total resistance of the circuit (2 marks)

$$\frac{1}{R_p} = \frac{1}{10} + \frac{1}{10} = \frac{2}{10}$$

$$R_p = 5\Omega$$

$$\begin{aligned} R_s &= R_p + 5 \\ &= 5 + 5 \\ &= 10\Omega \end{aligned}$$

$$\frac{1}{R_T} = \frac{1}{10} + \frac{1}{10} = \frac{2}{10}$$

$$R_T = 5\Omega$$

- b) Calculate the current and hence the voltage drop across the 10Ω resistor which is connected in parallel. (3 marks) ↓ marked on diagram.

$$R_T = 5\Omega$$


$$V_T = 120V$$

$$\begin{aligned} I_T &= \frac{V_T}{R_T} \\ &= \frac{120}{5} \\ &= 24A \end{aligned}$$

$$I_{10\Omega} = 6A \#$$

$$\begin{aligned} V_{10\Omega} &= I_{10\Omega} R_{10\Omega} \\ &= 6 \times 10 \\ &= 60V \# \end{aligned}$$

4.

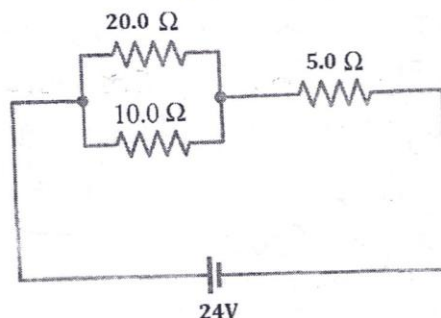

Calculate:

- a) The total resistance and the total current (2 marks)

$$\frac{1}{R_p} = \frac{1}{20} + \frac{1}{10} = \frac{3}{20}$$

$$R_p = \frac{20}{3}\Omega$$

$$\begin{aligned} R_T &= R_p + 5 \\ &= \frac{20}{3} + 5 \\ &= \frac{35}{3}\Omega \# \end{aligned}$$

$$R_T = \frac{35}{3}\Omega$$

$$V_T = 24V$$

$$\begin{aligned} I_T &= \frac{V_T}{R_T} \\ &= \frac{24}{\frac{35}{3}} \\ &= \frac{72}{35} A \# \end{aligned}$$

- b) The current and the voltage drop of the 5Ω resistor (2 marks)

5Ω is connected in series so

$$I_{5\Omega} = I_T = \frac{72}{35} \text{ A}$$

$$V_{5\Omega} = I_{5\Omega} R_{5\Omega} = \frac{72}{35} \times 5 = \frac{72}{7} \text{ V} \#$$

- c) The current and voltage drop of the 10Ω resistor (2 marks)

Method 1: Ratios

$$I_{10\Omega} = \frac{2}{3} \times I_T = \frac{2}{3} \times \frac{72}{35} = \frac{48}{35} \text{ A} \#$$

$$V_{10\Omega} = I_{10\Omega} R_{10\Omega} = \frac{48}{35} \times 10 = \frac{96}{7} \text{ V} \#$$


- d) The current and the voltage drop of the 20Ω resistor (2 marks)

Method 1: Ratios

$$I_{20\Omega} = \frac{1}{3} \times I_T = \frac{1}{3} \times \frac{72}{35} = \frac{24}{35} \text{ A} \#$$


$$V_{20\Omega} = I_{20\Omega} R_{20\Omega} = \frac{24}{35} \times 20 = \frac{96}{7} \text{ V} \#$$

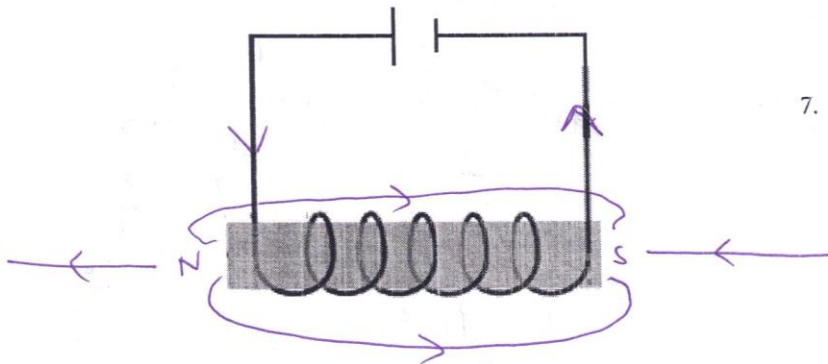5. Sketch the magnetic field surrounding the following: (2 marks each)
a)




Using Right hand Coil Rule

- b)

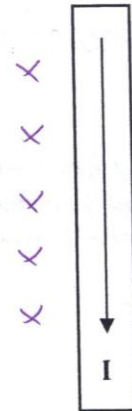

Using Right hand Grip Rule

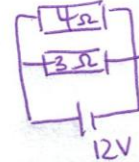6. Two resistors $R_1=4\Omega$ and $R_2=3\Omega$ are connected in parallel to a 12V power supply. What is the power generated by the power supply and the power dissipated in each resistor? (3 marks)



$$\frac{1}{R_T} = \frac{1}{3} + \frac{1}{4} = \frac{7}{12}$$

$$R_T = \frac{12}{7} \Omega$$

$$P_T = V_T I_T = V_T \cdot \frac{V_T}{R_T} = \frac{V_T^2}{R_T}$$

$$= \frac{12^2}{\frac{12}{7}} = 84 \text{ W} \#$$

$$P_{4\Omega} = \frac{V_{4\Omega}^2}{R_{4\Omega}} = \frac{12^2}{4} = 36 \text{ W} \#$$

$$P_{3\Omega} = \frac{V_{3\Omega}^2}{R_{3\Omega}} = \frac{12^2}{3} = 48 \text{ W} \#$$

7. How much energy (in kWh) does a 5kW heater use in 6 hours? (1 mark)

$$E = Pt = 5 \times 6 = 30 \text{ kWh}$$

$$\begin{cases} P = 5 \text{ kW} \\ t = 6 \text{ hrs} \end{cases}$$